

### Which Truth Tables Are the Same?

1)	B	A	F	2)	A	B	F
	0	0	0		0	0	0
	0	1	0		0	1	0
	1	0	1		1	0	1
	1	1	0		1	1	0

3)	B	A	F
	1	1	0
	1	0	1
	0	1	0
	0	0	0

1

### The Idea of Min Term / Product Term

X	Y	F	A	B	X	Y	Min Term
0	0	1	1	0	0	0	$X'Y'$
0	1	0	0	0	0	1	$X'Y$
1	0	0	0	0	1	0	$XY'$
1	1	1	0	1	1	1	$XY$

- Each row in a truth table represents a unique combination of variables
- Each row can be expressed as a logic combination specifying when that row combination is equal to a 1
- The term is called a MIN TERM or a PRODUCT TERM
- Thus  $F = A + B = X'Y' + XY$

2

### Truth Table with Two Inputs

- Two inputs X and Y; Output is F
- Logic Function:  
 $F = 1$  if and only if  $X = Y$

• Truth Table:

X	Y	F	Min Term
0	0	1	$X'Y'$
0	1	0	$X'Y$
1	0	0	$XY'$
1	1	1	$XY$

- Logic Expression:  
 $F = X'Y'.1 + X'Y.0 + XY'.0 + XY.1$   
 $= X'Y' + XY$

3

### Min / Product terms for more variables

XYZ	Min Term	XYZW	Min Term
000	$X'Y'Z'$	0000	$X'Y'Z'W'$
001	$X'Y'Z$	0001	$X'Y'Z'W$
010	$X'Y Z'$	0010	$X'Y'Z W'$
011	$X'Y Z$	0011	$X'Y'Z W$
100	$X Y'Z'$	0100	$X'Y Z'W'$
101	$X Y'Z$	0101	$X'Y Z'W$
110	$X Y Z'$	0110	$X'Y Z W'$
111	$X Y Z$	0111	$X'Y Z W$
		1000	$X Y'Z'W'$
		1001	$X Y'Z'W$
		1010	$X Y'Z W'$
		1011	$X Y'Z W$
		1100	$X Y Z'W'$
		1101	$X Y Z'W$
		1110	$X Y Z W'$
		1111	$X Y Z W$

4

### Truth Table with Three Inputs

- Three inputs X, Y, and Z; Output is F
- Logic Function:  
 $F = 1$  if and only if there is a 0 to the left of a 1 in the input

• Truth Table:

X	Y	Z	F	Min term
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	0	
1	1	1	0	

- Logic Expression:  
 $F =$

5

### Truth Table with Four Inputs

- Four inputs X, Y, Z, and W; Output is F
- Logic Function:  
 $F = 1$  if and only if number of variables with value 1 is more than the number of variables with value 0

• Truth Table:

XYZW	F
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	0
0111	1
1000	0
1001	0
1010	0
1011	1
1100	0
1101	1
1110	1
1111	1

- Logic Expression:  
 $F =$

6

### Canonical Sum-of-Product Expression

- A product (min) term is a unique combination of variables:
  - It has a value of 1 for only one input combination
  - It is 0 for all the other combinations of variables
- To write an expression, we need not write the entire truth table
- We only need those combinations for which function output is 1
- For example, for the function below:  $f = x'yz' + xy'z' + xyz$

x	y	z	f	Min term
0	0	0	0	
0	0	1	0	
0	1	0	1	$x'yz'$
0	1	1	0	
1	0	0	1	$xy'z'$
1	0	1	0	
1	1	0	0	
1	1	1	1	$xyz$

- This is called the Canonical Sum-of-Product (SOP) Expression

7

### Shorthand Notation for Canonical SOP

- We can also assign an integer to represent each input combination
- Thus the function produces a 1 for input combinations 2, 4, 7
- Therefore, the function can be written as  $f(x,y,z) = \sum m(2,4,7)$

x	y	z	f	Index for shorthand notation
0	0	0	0	0
0	0	1	0	1
0	1	0	1	2
0	1	1	0	3
1	0	0	1	4
1	0	1	0	5
1	1	0	0	6
1	1	1	1	7

8

### Max / Sum Terms

- A max (sum) term is also a unique combination of variables
  - However, it is opposite of a min term
  - It has a value of 0 for only one input combination
  - It is 1 for all the other combinations of variables
  - That is why it is called a max (sum) term
  - Each row in truth table has a max term corresponding to it
- Example, a max term  $(x+y+z)$  is 0 for combination  $xyz=000$  only

X	Y	Max Term
0	0	$X+Y$
0	1	$X+Y'$
1	0	$X'+Y$
1	1	$X'+Y'$

9

### Canonical Product-of-Sum Expression

- A function can also be written in terms of max terms
- The function is product of all max terms for which function is 0
- For example, the same function of three variable x, y, and z produces 0 for  $xyz=000, 011, 101$ , then
  - $F = (x+y+z).(x+y'+z').(x'+y+z')$
- This is called the Canonical Product-of-Sum (POS) Expression
- The function can also be written as  $F(x,y,z) = \prod M(0,3,5)$

X	Y	Z	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

$F = (F')'$   
 $= (x'y'z' + x'yz + xy'z)'$   
 $= (x+y+z).(x+y'+z').(x'+y+z')$

10

### Truth Tables and Logic Expression for Adder

A	B	C	X	Y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$X(A,B,C) = \sum m(1,2,4,7)$   
 $Y(A,B,C) = \sum m(3,5,6,7)$

$X(A,B,C) = \prod M( )$   
 $Y(A,B,C) = \prod M( )$

$$X = A'B'C + A'BC' + AB'C' + ABC$$

$$Y = A'BC + AB'C + ABC' + ABC$$

11

### Multiple Forms and Equivalence

- Canonical Sum-of-Product form
- Canonical Product-of-sum form
- How to convert one from other?
- Minterm expansion of X to minterm expansion of X'
- Just take the terms that are missing


$$X(A,B,C) = \sum m(1,2,4,7) \quad X'(A,B,C) = \sum m( )$$

- Maxterm expansion of X to maxterm expansion of X'
- Just take the terms that are missing

$$X(A,B,C) = \prod M( ) \quad X'(A,B,C) = \prod M( )$$

12

## Boolean Algebra

 

George Boole  
1815-1864

- An algebraic structure consists of
  - a set of elements {0, 1}
  - binary operators {+, ·}
  - and a unary operator { ' }
- Introduced by George Boole in 1854
- An effective means of describing circuits built with switches
- A powerful tool that can be used for designing and analyzing logic circuits

13

## Axioms of Boolean Algebra

- 1a:  $0 \cdot 0 = 0$   
1b:  $1 + 1 = 1$
- 2a:  $1 \cdot 1 = 1$   
2b:  $0 + 0 = 0$
- 3a:  $0 \cdot 1 = 1 \cdot 0 = 0$   
3b:  $1 + 0 = 0 + 1 = 1$
- 4a: If  $x=0$ , then  $x' = 1$   
4b: If  $x=1$ , then  $x' = 0$

14

## Single-Variable Theorems

- 5a:  $x \cdot 0 = 0$  Null
- 5b:  $x + 1 = 1$
- 6a:  $x \cdot 1 = x$  Identity
- 6b:  $x + 0 = x$
- 7a:  $x \cdot x = x$  Idempotency
- 7b:  $x + x = x$
- 8a:  $x \cdot x' = 0$  Complementarity
- 8b:  $x + x' = 1$
- 9:  $(x')' = x$  Involution

15

## Two- and Three-Variable Properties



- 10a:  $x \cdot y = y \cdot x$  Commutative
- 10b:  $x + y = y + x$
- 11a:  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$  Associative
- 11b:  $x + (y + z) = (x + y) + z$
- 12a:  $x \cdot (y + z) = x \cdot y + x \cdot z$  Distributive
- 12b:  $x + y \cdot z = (x + y) \cdot (x + z)$
- 13a:  $x + x \cdot y = x$  Absorption
- 13b:  $x \cdot (x + y) = x$
- 14a:  $x \cdot y + x \cdot y' = x$  Combining
- 14b:  $(x + y) \cdot (x + y') = x$
- 15a:  $(x \cdot y)' = x' + y'$  DeMorgan's Theorem
- 15b:  $(x + y)' = x' \cdot y'$
- 16a:  $x + x' \cdot y = x + y$  Another form of Absorption
- 16b:  $x \cdot (x' + y) = x \cdot y$

16

## Simplify Logic Function by Algebraic Manipulation

- $F = X'YZ + X'YZ' + XZ$   
 $= X'Y(Z + Z') + XZ$  by Distributive  
 $= X'Y(1) + XZ$  by Complementarity  
 $= X'Y + XZ$  by Identity

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

  



17

## Principle of Duality

- Dual:
  - A dual of a Boolean expression is derived by replacing  $\cdot$  by  $+$ ,  $+$  by  $\cdot$ , 0 by 1, and 1 by 0 and leaving variables unchanged
  - In general duality:  $f^D(x_1, x_2, \dots, x_n, 0, 1, +, \cdot) = f(x_1, x_2, \dots, x_n, 1, 0, \cdot, +)$
- Principle of Duality:
  - If any theorem can be proven, the dual theorem can also be proven.
  - A meta-theorem (a theorem about theorems)
- Examples:
  - Multiplication and factoring:
    - $(x + y) \cdot (x' + z) = x \cdot z + x' \cdot y$  and  $x \cdot y + x' \cdot z = (x + z) \cdot (x' + y)$
  - Consensus:
    - $(x \cdot y) + (y \cdot z) + (x' \cdot z) = x \cdot y + x' \cdot z$  and


18
  
### DeMorgan's Theorem in Terms of Logic Gates




19

### Using NAND to Implement SOP

 

20

### Using NOR to Implement POS

 

21

### Order of Precedence of Logic Operators

- From highest precedence to lowest: NOT, AND, OR
- We can use parenthesis to change the order


- Examples:

$f = X' + X.Y$  is the same as  
 $f = ((X') + (X.Y))$

$f = X.(Y+Z)$  is NOT the same as  
 $f = X.Y+Z$

22
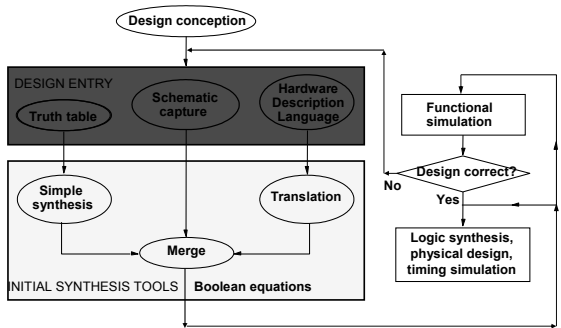
### A Typical CAD (Computer-Aided Design) System



23

### Verilog HDL

#### Popular Hardware Description Languages (HDLs):

- Verilog HDL
  - More popular with US companies
  - Similar to C / Pascal programming language in syntax
- VHDL
  - More popular with European companies
  - Similar to Ada programming language in syntax
  - More "verbose" than Verilog

#### Uses of Verilog:

- Synthesis
- Simulation
- Verification

24

## Verilog Syntax

- **Module / Signal names:**
  - Start with a letter
  - Follow by any sequence of letter, number, \_ and \$
  - Case sensitive
- **Comment by // or /\* \*/**
- **White spaces (SPACE, TAB, blank line) are ignored.**

```
// An example
module example1 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;

  and (g, x1, x2);
  not (k, x2);
  and (h, k, x3);
  or (f, g, h);
endmodule
```

```
// An example
module example1 (x1, x2, x3
, f);input x1, x2, x3;
output f;and (g, x1, x2);
not (k, x2);and (h, k, x3);
or (f, g, h);endmodule
```

25

## Multiplexer Circuit


$s x_1 x_2$	$f(s, x_1, x_2)$
000	0
001	0
010	1
011	1
100	0
101	1
110	0
111	1

Truth Table


$s$	$f(s, x_1, x_2)$
0	$x_1$
1	$x_2$

More compact truth-table representation

$$f = s'.x_1 + s.x_2$$

 


Circuit

 

Graphical symbol

26
 
## Structural Specification of Logic Circuit




```
module example1 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;

  and (g, x1, x2);
  not (k, x2);
  and (h, k, x3);
  or (f, g, h);
endmodule
```

endmodule

27
 
## Another Example of Structural Specification




```
module example2 (x1, x2, x3, x4, f, g, h);
  input x1, x2, x3, x4;
  output f, g, h;

  and (z1, x1, x3);
  and (z2, x2, x4);
  or (g, z1, z2);
  or (z3, x1, ~x3);
  or (z4, ~x2, x4);
  and (h, z3, z4);
  and (f, g, h);
endmodule
```

endmodule

28
 
## Behavioral Specification Continuous Assignment



```
// Structural Specification
module example1 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;

  and (g, x1, x2);
  not (k, x2);
  and (h, k, x3);
  or (f, g, h);
endmodule
```

```
// Behavioral Specification
module example3 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;


  assign f = (x1 & x2) | (~x2 & x3);
endmodule
```

Concurrent statement

endmodule

29
 
## Behavioral Specification Procedural (Sequential) Statement



```
module example5 (x1, x2, x3, f);
  input x1, x2, x3;
  output f;
  reg f;

  always @(x1 or x2 or x3)
  if (x2 == 1)
    f = x1;
  else
    f = x3;
endmodule
```

Declared as variable (register) if assigned a value in a procedural statement

Sensitivity list

always block

endmodule

30