 


Arithmetic

- Bits are just bits (no inherent meaning)
- Designing an ALU
 - It performs many functions
 - Each function may be implemented separately and then a result is selected based on need
 - A multiplexer is useful device for that



1

32-bit numbers

```

0000 0000 0000 0000 0000 0000 0000 0000two = 0ten
0000 0000 0000 0000 0000 0000 0001two = + 1ten
0000 0000 0000 0000 0000 0000 0010two = + 2ten
...
0111 1111 1111 1111 1111 1111 1110two = + 2,147,483,645ten
0111 1111 1111 1111 1111 1111 1111two = + 2,147,483,647ten
1000 0000 0000 0000 0000 0000 0000 0000two = - 2,147,483,648ten
1000 0000 0000 0000 0000 0000 0001two = - 2,147,483,649ten
1000 0000 0000 0000 0000 0000 0010two = - 2,147,483,646ten
...
1111 1111 1111 1111 1111 1111 1111 1101two = - 3ten
1111 1111 1111 1111 1111 1111 1110two = - 2ten
1111 1111 1111 1111 1111 1111 1111two = - 1ten

```

2

Two's Complement Operations

- Negating a two's complement number: invert all bits and add 1
 - remember: "negate" and "invert" are quite different!
- Converting n bit numbers into numbers with more than n bits:
 - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
 - copy the most significant bit (the sign bit) into the other bits

0010	->	0000 0010
1010	->	1111 1010
 - "sign extension"
 - To convert n bits to k bits k>n

3

Detecting Overflow

- No overflow when adding a positive and a negative number
- No overflow when signs are the same for subtraction
- Overflow occurs when the value affects the sign:
 - overflow when adding two positives yields a negative
 - or, adding two negatives gives a positive
 - or, subtract a negative from a positive and get a negative
 - or, subtract a positive from a negative and get a positive
- Consider the operations A + B, and A – B
 - Can overflow occur if B is 0 ?
 - Can overflow occur if A is 0 ?
- An exception (interrupt) occurs when overflow occurs
- Details based on software system / language
 - example: flight control vs. homework assignment
- Don't always want to detect overflow

4


An ALU (arithmetic logic unit)

- Let's build an ALU to support AND, OR, ADD, SUB and other functions
- we'll just build a 1 bit ALU, and use 32 of them

operation	op a b res
AND	0 0 0 0
OR	1 0 0 1
ADD	0 1 0 1
SUB	1 1 0 0
- Possible Implementation (sum-of-products):
 - How could we build a 1-bit ALU for add, and, and or?
 - How could we build a 32-bit ALU?

5

Building a 32 bit ALU

 


6

What about subtraction ($a - b$) ?

- Two's complement approach: just negate b and add.
- How do we negate?


- A very clever solution:

 

7

Supporting Other Function


- Can we figure out the idea?

 

8

A 32-bit ALU

 
- A Ripple carry ALU
- Two bits decide operation
 - Add/Sub
 - AND
 - OR
 - Other/LESS
- 1 bit decide add/sub operation
- A carry in bit
- Bit 31 generates overflow and set bit



9


Faster Adder: A 4-bit carry look-ahead adder

 - Generate g and p term for each bit
- Use g's, p's and carry in to generate all C's
- Use them to generate block G and P
- CLA principle is used recursively



10

Use principle to build bigger adders

 

11

Delays in carry look-ahead adders

- 4-Bit case**
 - Generation of g and p: 1 gate delay
 - Generation of carries (and G and P): 2 more gate delay
 - Generation of sum: 1 more gate delay
- 16-Bit case**
 - Generation of g and p: 1 gate delay
 - Generation of block G and P: 2 more gate delay
 - Generation of block carries: 2 more gate delay
 - Generation of bit carries: 2 more gate delay
 - Generation of sum: 1 more gate delay
- 64-Bit case**
 - 12 gate delays

12